

13 AC Circuits

- | | |
|-------------------------------------|---------------------------------------|
| 13.1 Introduction | 13.6 Power in AC circuit |
| 13.2 AC Generator | 13.7 LC Oscillations |
| 13.3 Average and RMS values | 13.8 Electric Resonance |
| 13.4 Phasors | 13.9 Sharpness of Resonance: Q-factor |
| 13.5 Different types of AC circuits | 13.10 Choke coil |

Quick Review

Alternating Signal

Voltage that vary with time periodically is called alternating voltage

The current driven by alternating voltage in a circuit is called alternating current

Peak value of an alternating current or voltage is the maximum value in either direction


70.7% of peak value is called root mean square value or **RMS value**

Caution

Ammeters and voltmeters always read the r.m.s. values.

Purely resistive circuit

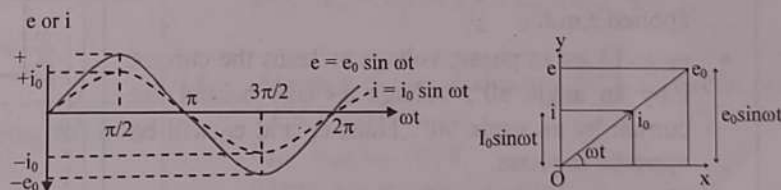
- Current and voltage are in phase
- It opposes A.C. as well as D.C.



Phasor Diagrams

Purely Inductive circuit

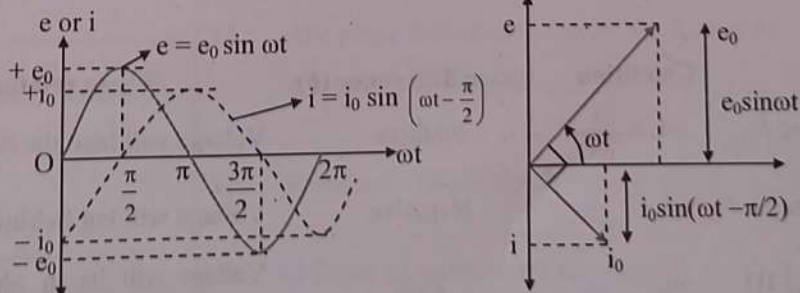- Current lags voltage by a phase of 90° .
- The effective resistance offered by the capacitor to the alternating current is called inductive reactance
- Average power consumed over one full cycle is zero.





Phasor Diagrams



Purely Capacitive circuit

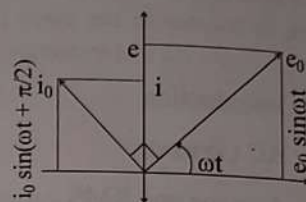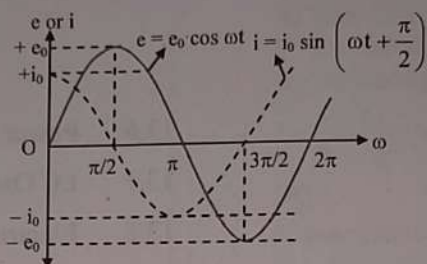- Current leads the voltage by a phase of 90° .
- The effective resistance offered by the capacitor to the alternating current is called capacitive reactance
- Average power consumed over one full cycle is zero.



Phasor Diagrams



➤ Resistance and reactance:

Sr. No.	Resistance	Reactance
i.	Equally effective for AC and DC.	Current is affected (reduced) but energy is not consumed (heat is not generated). The energy consumption by a coil is due to its resistive component.
ii.	Its value is independent of frequency of the AC	Inductive reactance (X_L) is directly proportional and capacitive reactance (X_C) is inversely proportional to the frequency of the AC.
iii.	Current opposed by a resistor is in phase with the voltage.	Current opposed by a pure inductor lags in phase while that opposed by a pure capacitor leads in phase by π^c over the voltage.

➤ LCR Series circuit:

- In series combination, the current I remains the same while the vector sum of potential difference across these components will be equal to the applied e.m.f.
- e_R and i are in phase, voltage e_L leads the current i by an angle 90° , voltage e_C lags behind the current by an angle 90° . Thus, e_L and e_C will be opposite in phase.
- The impedance (Z) of the circuit is,
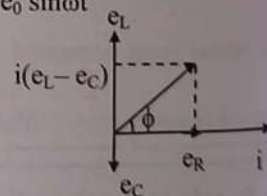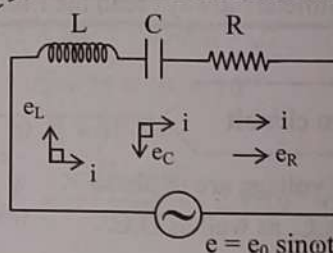
$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$



	Condition	Phase difference (ϕ)	Phase relation between voltage and current
Case I	$\omega L > \frac{1}{\omega C}$	Positive	Voltage will lead the current
Case II	$\omega L < \frac{1}{\omega C}$	Negative	Voltage will lag behind the current
Case III	$\omega L = \frac{1}{\omega C}$	Zero	Voltage will be in phase with the current. This state is called Resonance .

Electric Resonance

Resonance occurs when	X_L
Resonant frequency	$f =$
Impedance	Min
Current	Max

Graph

Wh
it,
reje
is n
call

Alternating e.m.f.

Alternating Current

Average value of

Average value of

R.M.S value of i

R.M.S value of i

Heat produced b

a complete cycl

For a pure indu

$$i = i_0 \sin \left[\omega t - \right]$$

Inductive reac



10. For a pure cap

$$i = i_0 \sin \left(\omega t + \right]$$

11. Capacitive re

Electric Resonance:

Chapter 13: AC Circuits

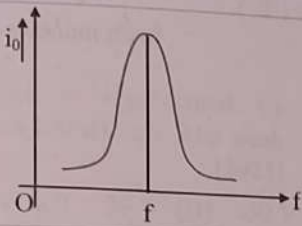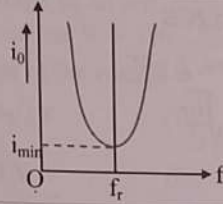	Series resonance	Parallel resonance
Resonance occurs when	$X_L = X_C$	$X_L = X_C$
Resonant frequency	$f = \frac{1}{2\pi\sqrt{LC}}$	$f = \frac{1}{2\pi\sqrt{LC}}$
Impedance	Minimum	Maximum
Current	Maximum	Minimum
Graph	 <p>When a number of frequencies are fed to it, it accepts only one frequency and rejects the other frequencies. The current is maximum for this frequency. Hence it is called acceptor circuit.</p>	 <p>When alternating current of different frequencies are sent through parallel resonant circuit, it offers a very high impedance to the current of the resonant frequency and rejects it but allows the current of the other frequencies to pass through it, hence called a rejector circuit.</p>

Formulae

1. Alternating e.m.f.: $e = e_0 \sin \omega t$
2. Alternating Current: $i = i_0 \sin (\omega t + \alpha)$
3. Average value of current: $i_{av} = 0.637 i_0$
4. Average value of e.m.f.: $e_{av} = 0.637 e_0$
5. R.M.S value of induced e.m.f.: $e_{rms} = \frac{e_0}{\sqrt{2}}$
6. R.M.S value of induced current: $i_{rms} = \frac{i_0}{\sqrt{2}}$
7. Heat produced by a sinusoidally varying AC over a complete cycle: $H = R(i_{rms})^2 \cdot \frac{2\pi}{\omega}$
8. For a pure inductor circuit:
 $i = i_0 \sin \left[\omega t - \frac{\pi}{2} \right]$, where, $i_0 = \frac{V_0}{\omega L}$
9. Inductive reactance: $X_L = \frac{e_{rms}}{i_{rms}} = \omega L = 2\pi fL$
10. For a pure capacitor circuit:
 $i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$, where, $i_0 = \frac{V_0}{1/\omega C}$
11. Capacitive reactance: $X_C = \frac{e_{rms}}{i_{rms}} = \frac{1}{\omega C} = \frac{1}{2\pi fC}$
12. Impedance:
 - In LCR circuit,
 $Z = \frac{e_{rms}}{i_{rms}} = \sqrt{R^2 + (X_L - X_C)^2}$
 - In LR circuit, $Z = \sqrt{R^2 + X_L^2}$
 - In CR circuit, $Z = \sqrt{R^2 + X_C^2}$
13. Average power in AC circuit with resistance only: $P_{av} = \frac{e_0 i_0}{2} = \frac{e_0}{\sqrt{2}} \times \frac{i_0}{\sqrt{2}} = e_{r.m.s} \times i_{r.m.s}$
14. Average power dissipated in A.C circuit with LCR in series:
 $P_{av} = e_{rms} i_{rms} \cos \phi$
where, $\cos \phi$ = power factor
15. Power factor: $\cos \phi = \frac{\text{True power}}{\text{Apparent power}} = \frac{R}{Z}$
16. The phase difference between X_L , X_C and R :
 $\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$
17. Resonance frequency: $f_r = \frac{1}{2\pi\sqrt{LC}}$
18. Q factor of series resonant circuit:
 $Q = \frac{\omega_r}{\omega_2 - \omega_1} = \frac{\omega_r}{2\Delta\omega} = \frac{\text{Resonant frequency}}{\text{Bandwidth}}$



Shortcuts

- Average value of $\sin^2 \omega t$ over complete cycle is $\frac{1}{2}$.
- Mnemonics
 - In inductive ('L') circuits, voltage ('E') leads current ('I').
Mnemonic: ELI
 - In capacitive ('C') circuits, current ('I') leads voltage ('E').
Mnemonic: ICE
- At resonance, $Z = R$

$$X_L = X_C = \sqrt{\frac{L}{C}}$$

$$I = \frac{V}{R}$$
- The quality factor of series resonant circuit is also defined as the ratio of voltage drop across capacitor or inductor to the voltage drop across the resistor.
 i.e., $Q = \frac{\omega_r L}{R}$ where, ω_r = resonant frequency

Voltage leads current

ELI

In an inductor

Current leads voltage

ICE

In a capacitor

m.s. current in an
 of current $\frac{1}{200}$
 zero is (frequ
 $\frac{\pi}{2} = 1$)
 3 A
 $3\sqrt{2}$ A
 alternating voltage
 $= 80 \sin(100\pi t) \cos$
 is
 20 V (B) 40 V
 instantaneous val
 is given by $i =$
 ve a value of 25 A
 in $30^\circ = 0.5$)
 1