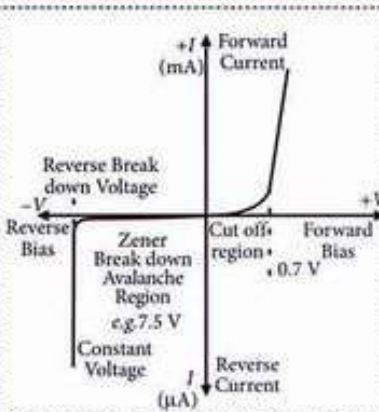


TYPES OF SEMICONDUCTORS

INTRINSIC SEMICONDUCTORS

The pure semiconductors have thermally generated current carriers. Here, $n_e = n_h = n_i$



APPLICATIONS OF DIODE

- **Diode as a rectifier**
 - Half wave rectifier
 - Full wave rectifier
- **Zener diode as a voltage regulator.**
- **Photo diode** for detecting light signals.
- **LED:** light emitting diode.
- **Solar cells:** Generates emf from solar radiations.

EXTRINSIC SEMICONDUCTORS

The semiconductor whose conductivity is mainly due to doping of impurity.

p-type semiconductor

- Doped with trivalent atom.
- Here, $n_h \gg n_e$

n-type semiconductor

- Doped with pentavalent atom.
- Here, $n_e \gg n_h$

SEMICONDUCTOR DIODE

p-n junction diode: A p-type semiconductor is brought into contact with an n-type semiconductor such that structure remains continuous at boundary.

BIASING CHARACTERISTICS

Forward bias characteristic

- Width of depletion layer decreases
- Effective barrier potential decreases
- Low resistance at junction
- High current flow of the order of mA.

Reverse bias characteristic

- Width of depletion layer increases
- Effective barrier potential increases
- High resistance at the junction
- Low current flow of the order of μA .
- Reverse break down occurs at a high reverse bias voltage.

JUNCTION TRANSISTOR


A semiconductor device possessing fundamental action of transfer resistor.

Junction transistors are of two types

- **n-p-n transistor:** A thin layer of p-type semiconductor is sandwiched between two n-type semiconductors.
- **p-n-p transistor:** A thin layer of n-type semiconductor is sandwiched between two p-type semiconductors.

There are three configurations of transistors

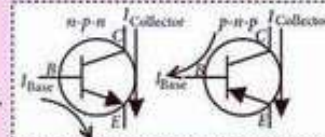- CB (Common Base)
- CE (Common Emitter)
- CC (Common Collector).



Transistor characteristics


- Input resistance $(r_i)_{(CE)} = \left(\frac{\Delta V_{BE}}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$
- Output resistance $(r_o)_{(CE)} = \left(\frac{\Delta V_{CE}}{\Delta I_C} \right)_{I_B = \text{constant}}$
- Current amplification factor $\beta_{ac} = \left(\frac{\Delta I_C}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$ and $\alpha_{ac} = \left(\frac{\Delta I_C}{\Delta I_E} \right)_{V_{CB} = \text{constant}}$

APPLICATIONS OF TRANSISTOR

- **Transistor as an Amplifier**
 - Its operating voltage is fix in active region.
 - Voltage gain,

$$A_v = \frac{V_o}{V_i} = -\beta_{ac} \frac{R_{out}}{R_{in}}$$

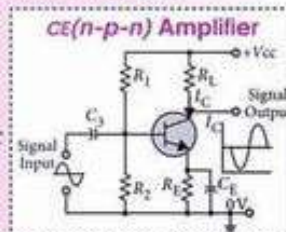- Power gain, $A_p = A_v \times \beta_{ac}$
- **Transistor as a Switch**
- **Transistor as an Oscillator**



DIGITAL ELECTRONICS AND LOGIC GATES

VARIOUS TYPES OF LOGIC GATE

AND Gate

Output is high only when both inputs are high.

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$Y = A \cdot B$

OR Gate

Output is high if any one or both inputs are high.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$Y = A + B$

NOT Gate

It just inverts the input signal.

A	Y
0	1
1	0

$Y = \bar{A}$

NAND Gate

An AND Gate followed by a NOT Gate.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

$Y = \overline{A \cdot B}$

NOR Gate

An OR Gate followed by a NOT Gate.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$Y = \overline{A + B}$